

Registration No: -

2	2	0	1	2	0	2	4	5	5
---	---	---	---	---	---	---	---	---	---

Total Number of Pages: 03

B.Tech / 22IT3ES02T

3rd Semester Regular Examination: 2023-24

DIGITAL LOGIC DESIGN

BRANCH: IT

Time: 3 Hours

Max Marks: 100

Q Code: P132


Answer Question No.1 (Part-I) which is compulsory, any EIGHT from Part-II and any TWO from Part-III.

The figures in the right hand margin indicate marks.

### Part-I


Q No. Q1	CO	Level	Short Answer Type Questions (Answer All-10)	(02x10)
a)	1	1	Which logic gate is called universal logic gate and why it is called universal logic gate?	2
b)	1	1	Which logic gate is said to be equivalence gate? Write its truth table.	2
c)	2	3	Prove that: $AB + A'C + BC = AB + A'C$ using Boolean algebra theorems and postulates	2
d)	2	3	<div style="text-align: center;"> </div>	2
e)	2	3	Find the simplified SOP from above K-Map.	2
f)	2	3	Design 4x1 MUX using 2X1 MUXes [use block diagram of 2x1 MUX]	2
g)	3	2	Let a Gray code is: 10011010 Find the Binary equivalent of the above Gray code.	2
h)	3	2	State the characteristic equation of T flip-flop.	2
i)	4	2	What is the difference between SR flip-flop and JK flip-flop?	2
j)	4	3	What is race-around condition?	2
			How many address lines required to design a 512KB memory?	2

## Part-II

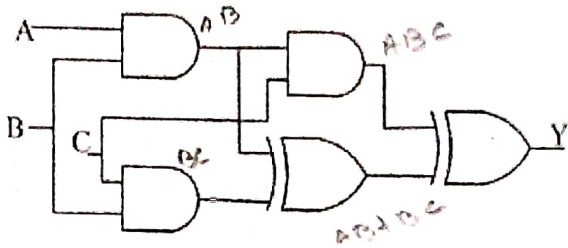
Q No. Q2	CO	Level	Focused-Short Answer Type Questions- (Answer Any Eight out of Twelve)	(06x08)
a) ✓	1	3	Perform $(23_{10}) - (-14_{10})$ using 2's complement method.	6
b)	1	3	For the circuit shown below, find the truth table and write the Boolean function of Y.	6
c)	1			6
d) ✓	2	3	Simply the following function [in the form of SOP] using 4 variable K-Map $F(w,x,y,z) = \pi M(0,2,3,8,9,10,11,15)$	6
e) ✓	2	3	Construct Full Adder using two Half Adders and with an additional logic gate.	6
f) ✓	2	3	Design 3 bit Binary to Gray code converter	6
g) ✓	2	3	Implement the given function using 8X1 MUX $F(A,B,C,D) = \sum m(1,4,5,7,9,12,13)$	6
h) ✓	3	3	Derive Characteristic Table and Characteristic Equation of SR flip-flop	6
i) ✓	3	2	Draw and explain the operation of positive edge triggered D flip-flop	6
j) ✓	3	4	Show that a JK flip-flop can be converted to T flip-flop. Design it with the help of necessary tables and diagrams	6
k)	4	2	Draw the diagram of 1-bit SRAM cell and explain its operation.	6
l)	4	2	Differentiate between SRAM and DRAM	6

## Part-III

Q No.	CO	Level	Long Answer Type Questions (Answer Any Two out of Four)	(02x16)
Q3	a)	1	Reduce the following expressions to indicated number of literals: i. $(A' + C)(A' + C')(A + B + C'D)$ to four literals. ii. $(A'B(D' + C'D) + B(A + A'CD))$ to one literal.	8
	b)	1	Verify algebraically that the circuit shown in the below figure implements the following Boolean function, $F = \overline{C}(\overline{A} + \overline{B}) + \overline{D}$ . Also represent F in canonical SOP form.	8

 

Q4	a)	2	3	A multiplier is a combinational logic circuit which multiplies two numbers in binary form. Design a 2-bit multiplier that multiplies two 2-bit numbers.	8
	b)	2	3	Design 4-bit Binary Parallel Adder using Full Adders.	8
Q5	a)	3	4	Design 3-bit synchronous DOWN counter. Draw the neat diagram of the counter.	8
	b)	3	4	Design the sequential logic circuit using T flip-flops which is described by the following state diagram	8

 

Q6	a)	3	3	Draw and explain the operation of SISO shift register. Find sequence of states of a Johnson Counter if the initial state is $(1000)_2$ .	4+4
	b)	4	3	A decoder is used in memory decoding. Explain with the help of suitable example.	8